
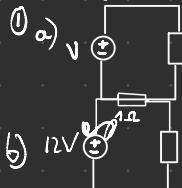


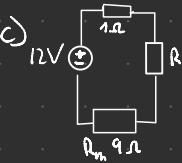


① a) 
 $\omega = k \cdot i \Rightarrow i = \frac{\omega}{R}$
 $V = \frac{\omega R}{k} = \frac{10 \cdot 9}{20} = 4,5 \text{ V}$


b) 
 $\omega = k \cdot \frac{V}{R} = 20 \cdot \frac{12}{10} = 24 \text{ rpm}$


c) 
 $R_s = R_{tot} = \frac{kV}{\omega} = \frac{20 \cdot 12}{12} = 20$
 $R_L = R_{tot} - R_m - R_i = 20\Omega - 9\Omega - 1\Omega = 10\Omega$


d) 
 $i = \frac{\omega t}{R} = \frac{12}{20} = 0,6 \text{ A}$
 $V = iR_p = 0,6A \cdot 9\Omega = 5,4 \text{ V}$
 $V_1 = 12 \text{ V} - 5,4 \text{ V} = 6,6 \text{ V}$
 $I_1 = \frac{6,6 \text{ V}}{1\Omega} = 6,6 \text{ A}$
 $I_{R_p} = 6,6 \text{ A} - 0,6 \text{ A} = 6 \text{ A}$
 $R_p = \frac{5,4 \text{ V}}{6,6 \text{ A}} = 0,9 \Omega$

e) V_i ser ut strømmen gjennom Lauraas løsning
er høyere og gir dermed kortere levetid

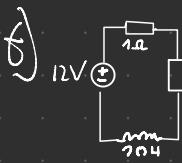f) 
 $I = \frac{12 \text{ V}}{10\Omega} = 1,2 \text{ A}$
 $i = \frac{\omega t}{R} = \frac{20}{20} = 1$
 $\tau = \frac{L}{R} = \frac{20 \text{ H}}{10\Omega} = 2$
 $i(t) = 1,2 - 1,2 e^{-\frac{t}{\tau}}$
 $t_c = -\ln\left(\frac{1}{2}\right) \cdot \tau = 3,58 \text{ s}$

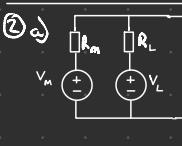② a) 
 $V_{tot} = \frac{V_m \cdot R_L \cdot R_F}{R_m R_L + R_m R_F + R_L R_F} + \frac{V_L \cdot R_m \cdot R_F}{R_m R_L + R_m R_F + R_L R_F}$
 $V_{tot} = \frac{R_F}{R_m R_L + R_m R_F + R_L R_F} (R_m V_L + R_F V_m)$

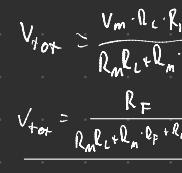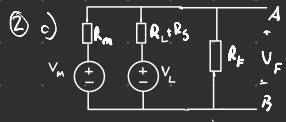b) 
 $V_{tot} = \frac{V_m \cdot R_L \cdot R_F}{R_m R_L + R_m R_F + R_L R_F} + \frac{V_L \cdot R_m \cdot R_F}{R_m R_L + R_m R_F + R_L R_F}$
 $V_{tot} = \frac{V_L \cdot R_m \cdot R_F}{R_m R_L + R_m R_F + R_L R_F}$



$$\frac{V_L \cdot R_m \cdot R_F}{R_m \cdot R_F + R_m \cdot R_F + R_F \cdot R_F + R_F \cdot R_F} = \frac{1}{2} \frac{V_L \cdot R_m \cdot R_F}{R_m \cdot R_F + R_m \cdot R_F + R_F \cdot R_F}$$


$$R_F \cdot R_F + R_m \cdot R_F + R_F \cdot R_F + R_F \cdot R_F = 2(R_m \cdot R_F + R_m \cdot R_F + R_F \cdot R_F)$$

$$R_S (R_{\text{out}} + R_F) = R_m \cdot R_F + R_m \cdot R_F + R_F \cdot R_F$$

$$R_S = \frac{R_m \cdot R_F + R_m \cdot R_F + R_F \cdot R_F}{(R_m + R_F)} = R_F + \frac{R_m \cdot R_F}{R_F + R_m}$$

3)a) Han trenger noks styresignaler når det er 8 ulike signaler. Nå har han $2^3 = 8$, han trenger 24 styre signaler


b)

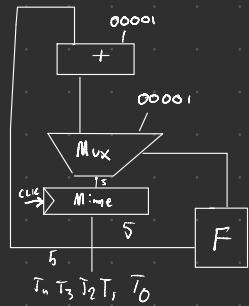

$$A_1 = T_4 + T_3 + T_2 + T_1 + T_0$$

$$A_3 = T_4 + T_3 + T_2 + T_1 + T_0$$

$$A_{24} = T_4 \cdot T_3$$

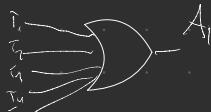

$$T_4 = 0 - A_{24}$$

$$\begin{array}{c|ccc|ccc} & T_4 & T_3 & T_2 & T_1 & T_0 & A_1 & A_3 & A_{24} \\ \hline 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 1 & 1 & 1 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & 1 & 1 & 0 \\ 0 & 0 & 1 & 0 & 0 & 1 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 & 1 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 1 & 1 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 1 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \end{array}$$

